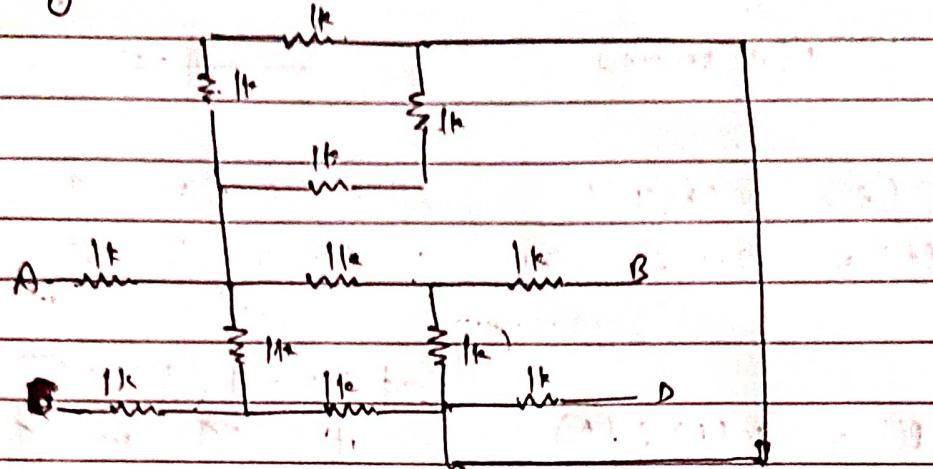


Basic - Electronic  
Assignment - 1

1


DATE

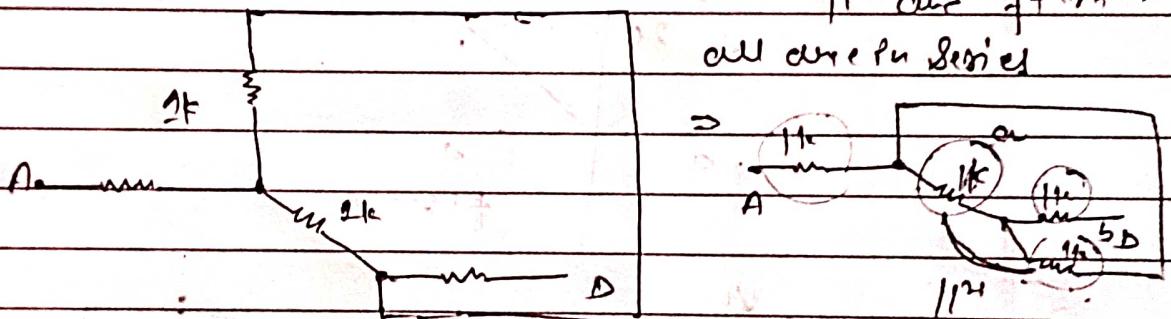- Q. 1 Find equivalent resistance between the points A and D in the given below circuit



SHORT CIRCUIT

C and b are in  
1<sup>st</sup> and 2<sup>nd</sup> series  
all are in series



$$( \text{Equivalent Resistance} ) \Rightarrow R_e = \frac{1 + 1}{2(1 + 2)} = \frac{2}{3} \Rightarrow R_e' = \frac{1}{2}$$

$R_e = R_1 + R_2 + R_3$  (Series Connection)


$R_e = R \left( \frac{1}{n} \right)^2$  - Equivalent Resistance

- Q. 2 The voltage  $v(t)$  and current  $i(t)$  through an electrical circuit element is given below. Draw the absorbed power in each and every cases (for all time period)

#

PAGE

(2)

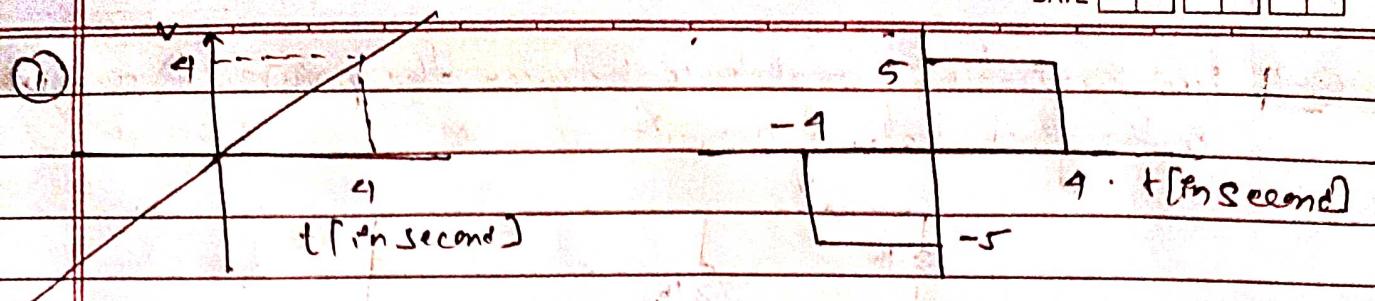T(t) [Phonab]  
DATE

$$P(t) = v(t)I(t)$$

at  $t=4$   $P(t) = 4 \times 4 = 20$

$v = 4$



$t = 4$   $I = 5$

$$P(t) = v(t)I(t)$$

at  $t=-4$   $v = -4$

$t = -4$ ,  $v = -4$


$$P(t) = -4 \times -5 = +20$$

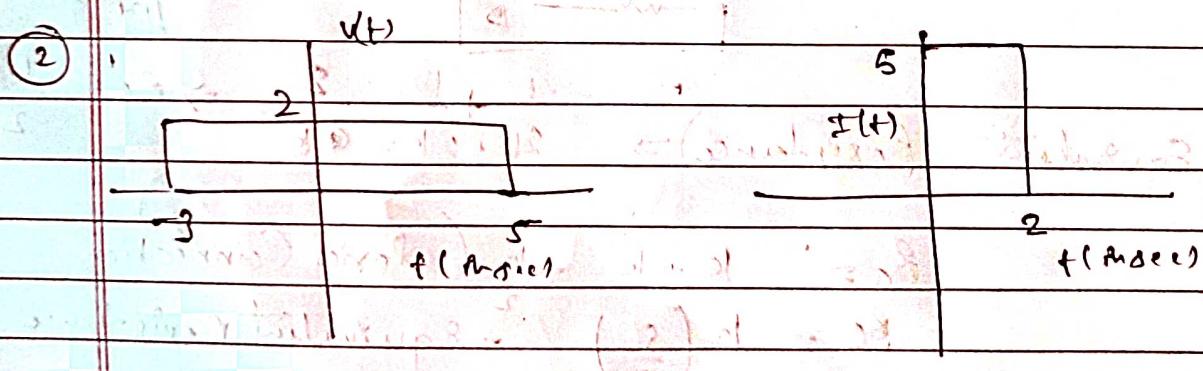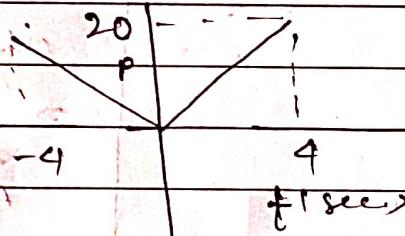

$$P(t) = v(t)I(t)$$



$v(t)$  Constant in between (0 to 2) sec

$v(t) = 10$  m/sec

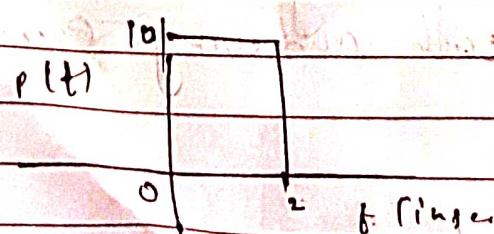


3

DATE

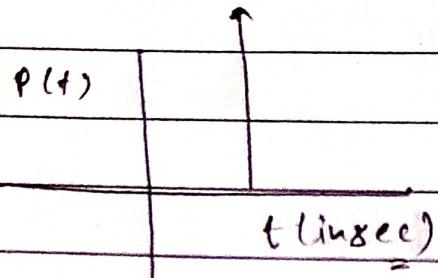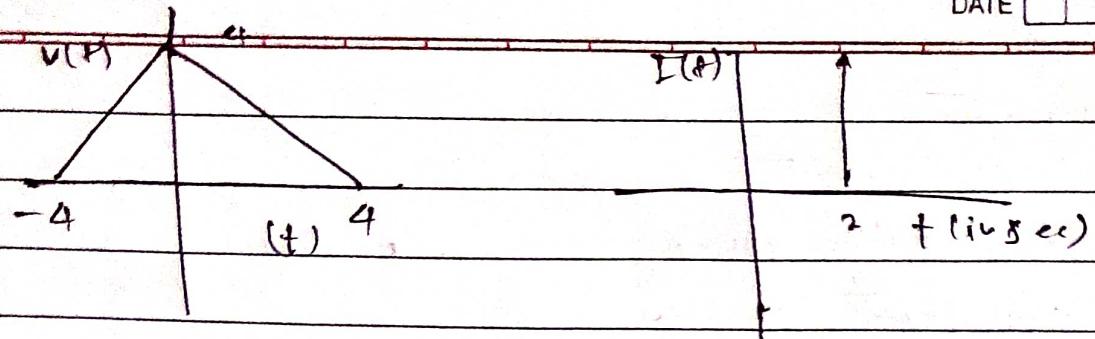

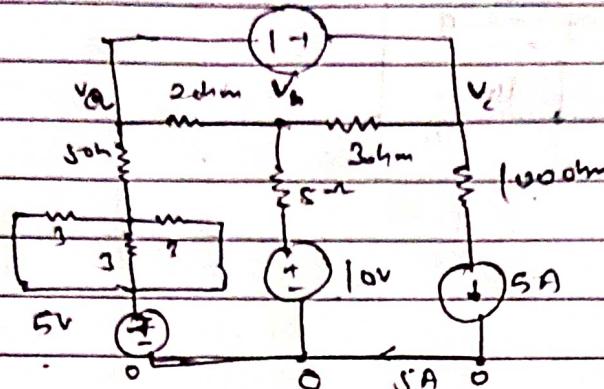Q. 6 In the given following circuit find the value of node voltages  $V_a$ ,  $V_b$ , and  $V_c$  with the help of KVL, KCL and Ohm's law.



Using KCL at node 1 :

$$\frac{V_b - V_a}{2} + \frac{V_b - V_c}{3} + \frac{V_b - 10}{5} = 0 \Rightarrow 31V_b - 15V_a - 15V_c = 0 \quad (1)$$

Using KVL in loop II :

$$+2 + \frac{V_a - V_b}{2} + \frac{V_b - V_c}{3} = 0$$

$$\text{Or } 12 + 3V_a - 3V_b + 2V_b - 2V_c = 0$$

$$3V_a - 8V_b - 2V_c = 12 \quad (2)$$

$$\rightarrow 5 + \frac{5 - V_a}{6} + \frac{10 - V_b}{5}$$

$$\Rightarrow V_a + V_b = -6.5 \quad (3)$$

Take eq<sup>n</sup> (1) and (2)

Subtracting (1) from (2)

$$15V_a - 5V_b - 10V_c = 60$$

$$+ 31V_b - 15V_a - 10V_c = 0$$

$$(30V_a + 36V_b = 60)$$

(5)

DATE    

$$30v_a + 36v_b = 60$$

$$5v_a + 6v_b = 10$$

$$v_a + v_b = -6.5$$

$$v_b = 33.5$$

$$v_a = \frac{10 - 6v_b}{5} = \frac{10 - 6(-6.5)}{5} = 400V$$

$$v_c = 10 - 5(33.5) - 60 = -233.5V$$

$$v_b = 33.5$$


$$v_a = 400V$$

$$v_c = -233.5$$

$$+v_b = 33.5$$



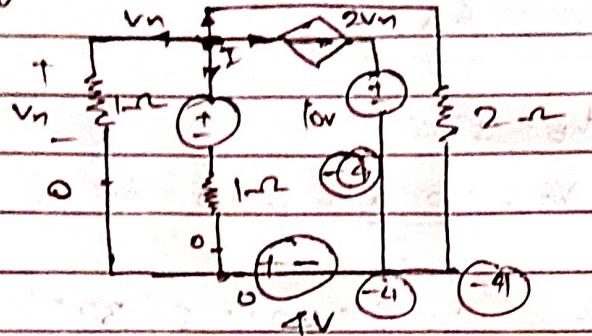Q. 4 Find the value of ' $V_n$ ' with the help of nodal analysis in the given below circuit.



Use nodal voltage of I


$$\frac{V_n - 0}{1} + \frac{2V_n - V_n + 4}{2} + \frac{V_n - 9}{1} = 0$$

$$\text{or } V_n + 2V_n + \frac{V_n}{2} + 2 - V_n - 9 = 0$$

$$\frac{9}{2} V_n = 9$$

$$V_n = 4 \text{ volt}$$

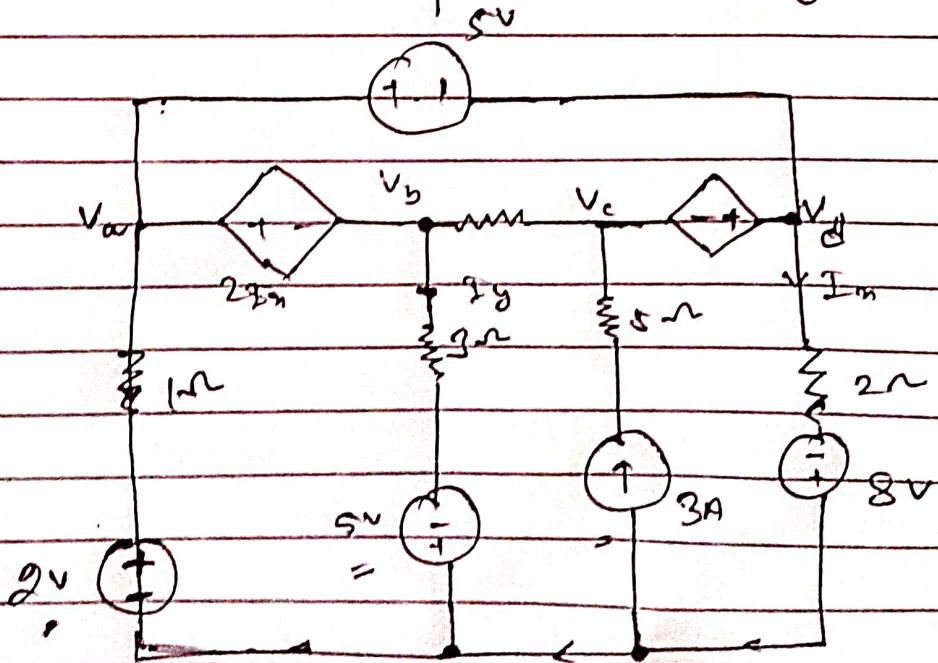Q. 5 In the given following circuit find the node voltage  $V_{an}$ ,  $V_b$ ,  $V_c$  and  $V_d$  with the help of nodal analysis.




Analyzing loop law under loop

$$= 5 + 2I_n - 8 - 2 + I_n + I_y = 0$$

$$\Rightarrow 3I_n + I_y = 8$$

$\Rightarrow$

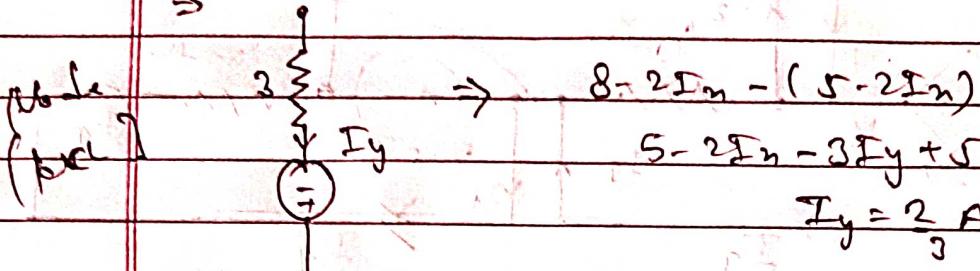

$$8 - 2I_n - (5 - 2I_n)$$

$$5 - 2I_n - 3I_y + 5 = 8 \Rightarrow I_n$$

$$I_y = \frac{2}{3} A$$

$$8 - 2I_n$$

$$I_n = \frac{8 - I_y}{3} = \frac{8 - 2}{3}$$

$$\Rightarrow \frac{22}{9}$$

$$V_a = 5V$$


$$V_b = 5 - 2I_n = (5 - 4 \times \frac{2}{3})V = 13 \frac{1}{3} V$$

$$V_c = -3I_y = -3 \times \frac{2}{3} = -2V$$

$$V_d = 0V$$

$V_a = 5V$
$V_b = 13 \frac{1}{3} V$
$V_c = -2V$
$V_d = 0V$

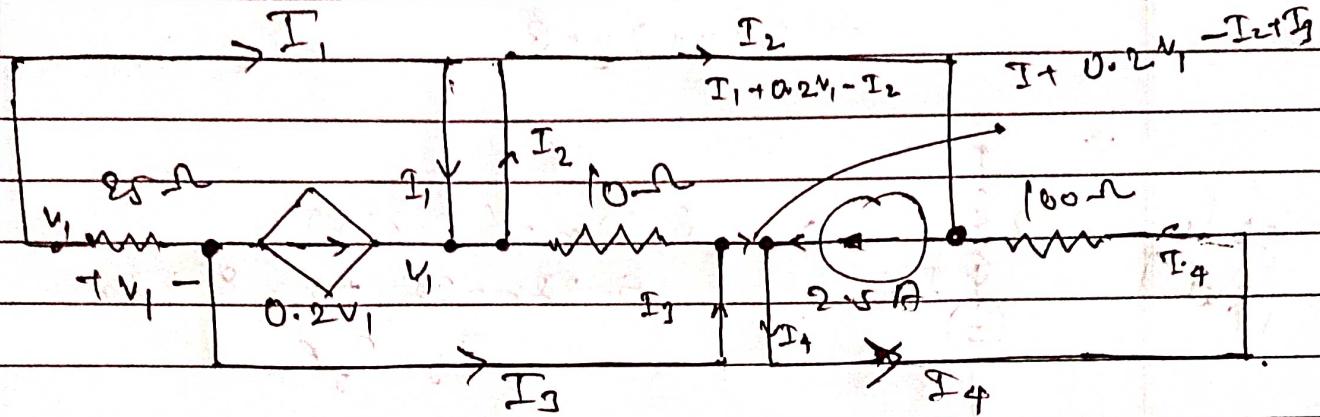Q15 In the given following circuit, find the value of current  $I_1, I_2, I_3$  &  $I_4$  with the help of nodal analysis.



$$\Rightarrow I_1 + 0.2V_1$$

$$-I_2 + I_3$$

$$+ 2.5$$

$$\Rightarrow I_1 + 0.2V_1 - I_2 + I_3 + 2.5 = I_4$$

$$\begin{vmatrix} V_1 & 0 & 0 & 0 \\ 0 & V_2 & -1 & 0 \\ 0 & -1 & V_3 & 0 \\ 0 & 0 & 0 & V_4 \end{vmatrix}$$